


Digital Logic: From Gates to Functions and Memory

Professor Bob Brown – Kennesaw State University

Bob.Brown@Kennesaw.edu

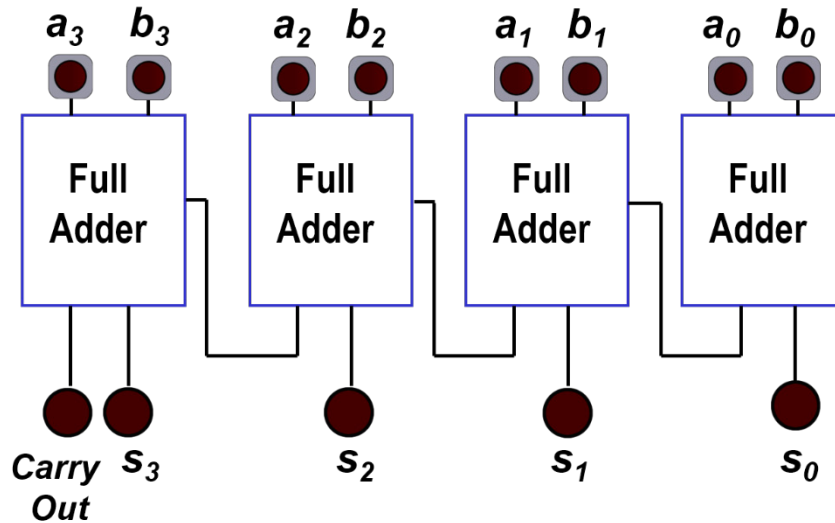Exercise: Build a 5-bit Adder

The diagram shows a 4-bit adder. Extend the design to build a **5-bit adder**. Space your adder chips about one gate-width apart so that you have room to work.



Test these values and a few others. With eight inputs, there are $2^8 = 256$ possible input combinations. Testing them all in class is not a good use of time.

| A ₄ | B ₄ | A ₃ | B ₃ | A ₂ | B ₂ | A ₁ | B ₁ | A ₀ | B ₀ | S ₃ | S ₂ | S ₁ | S ₀ | C _o |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | | | | | |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | | | | | |
| | | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | | | | | |
| 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | | | | | |
| | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | |


Exercise:

If a particular full adder requires one nanosecond to complete its computation, how long will a 32-bit ripple-carry adder take to complete an addition? A 64-bit ripple-carry adder?

Another Gate


The NOR gate looks like a NOT gate with a circle at the output. The circle is called a negation bubble. NOR is an abbreviation for NOT-OR. Compare the truth table to that of the OR gate.


| A | B | A NOR B |
|---|---|---------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

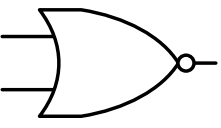

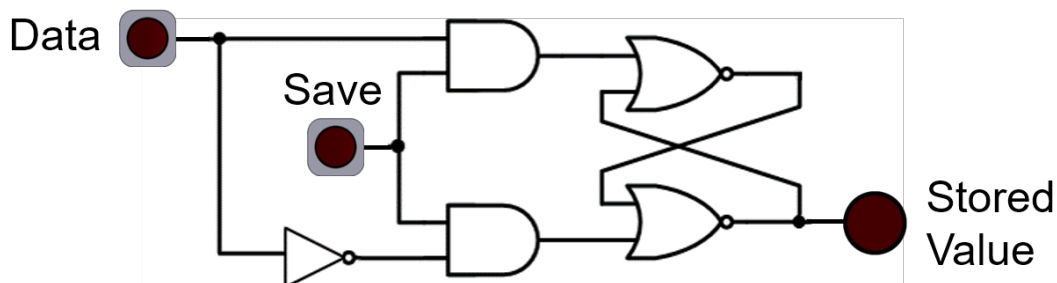Exercise:

Build a clocked D-Latch. Use pushbuttons for the inputs marked “Data” and “Save.”

When you have your D-latch working, delete the pushbutton marked “Save” and replace it with the Digital Works clock generator. It’s in the parts bar, just to the left of the pushbutton, and looks like this: 



If we were building an actual computer, the computational circuits, like the adder, would have to finish their work within the time of each clock cycle. To make the clock faster, all the other circuits must also be made faster, or we would risk storing data before the computations were complete.

Note: The D-latch is transistor memory. Computer designers use transistor memory when speed is needed. The RAM is generally dynamic RAM, or DRAM. It uses charge storage to store bits. It’s somewhat slower, but much less expensive than transistor memory.



College of Computing and Software Engineering

Copyright © 2018 by Kennesaw State University

Creative Commons 4.0 Attribution Non-commercial License

